

940

Register No.:

April 2024

*Time - Three hours*  
(Maximum Marks: 100)

- [N.B. 1. Answer all questions under Part-A. Each question carries 3 marks.  
2. Answer all the questions either (A) or (B) in Part-B. Each question carries 14 marks.]

PART - A

1. Mention the characteristics of op-amp.
2. Draw the pin diagram of op-amp IC 741.
3. Define resolution and settling time of DAC.
4. Mention the different types of IC voltage regulator.
5. State De-Morgan's theorem.
6. Construct the logic diagram for the equation  $Y=A'BC+ABC+AB'C$ .
7. Define Asynchronous counter.
8. Write the characteristic equation of JK flip flop.
9. Differentiate static RAM and dynamic RAM.
10. Expand DDR RAM, EEPROM and SDRAM.

[Turn over.....

PART - B

11. (a) (i) Explain zero crossing detector using op-amp. (7)  
(ii) Briefly explain about integrator.(7)

(Or)

- (b) Explain about RC low pass active filter.

12. (a) With the diagram explain dual slope ADC.

(Or)

- (b) With the diagram explain monostable multivibrator using IC555.

13. (a) Simplify the following function using K-map  $F = \sum(3,4,5,6,7,8,9,12,13)$  and construct its logic diagram.

(Or)

- (b) Design and Construct a full adder circuit.

14. (a) (i) What is the difference between a multiplexer and de-multiplexer? (4)

- (ii) Explain the operation of a 4 to 1 multiplexer.(10)

(Or)

- (b) Define mod-N counter. With the logic diagram explain the operation of mod-7 counter.

15. (a) Explain the working principle of bipolar RAM cell.

(Or)

- (b) Explain EPROM and EEPROM organization with necessary diagrams.

-----